
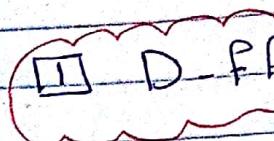


Flip Flops

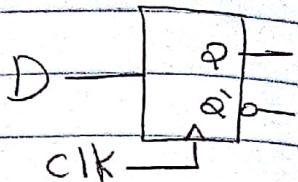


\Rightarrow (Delay flip flop)

$$Q(t+1) = D$$




\Rightarrow (Set/Reset flip flop)

$$Q(t+1) = S + R'Q$$

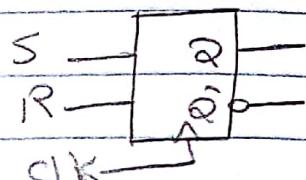


\Rightarrow (Toggle flip flop)

$$Q(t+1) = T \oplus Q$$

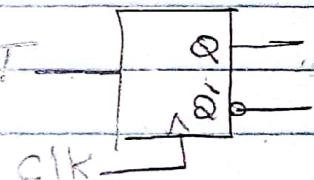

\Rightarrow JK - FF

$$Q(t+1) = JQ' + K'Q$$

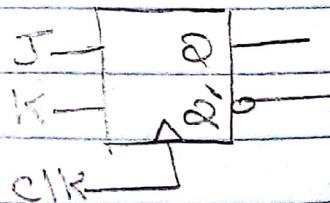

$$Q(t+1)$$

\hookrightarrow is called

- Characteristic equation or
- Next state equation or
- State equation

Q5.3)

Show that, the characteristic equation for the Complement output of a JK flip flop is:

$$Q'(t+1) = J'Q + KQ$$

Answer:

(JK.) Q^* الباقي من Q

$$Q^* \text{ or } Q(t+1) = JQ + KQ$$

الباقي من $(K \cdot \text{not } J)$ هو المخرج \bar{Q}

	KQ	KQ	KQ	KQ	JQ	JQ
J	0	1	1	0	0	0
J	1	0	0	1	1	0

$(Q^* \text{ for } JK)$ or (The Complement) الباقي من الباقي

$$Q'(t+1) = J'Q + KQ$$

~~or implement~~

~~How to Construct Any Flip Flop From another one?~~

~~Using D flip flop with its own inputs and outputs~~

~~Ex 1:~~


How to implement the (JKFF) by using (DFF) ?

Ans.


→ The input to the D Flip Flop will be
The equation of The (JKFF) is

~~How to construct~~

$$Q(t+1) = J \bar{Q} + K Q$$

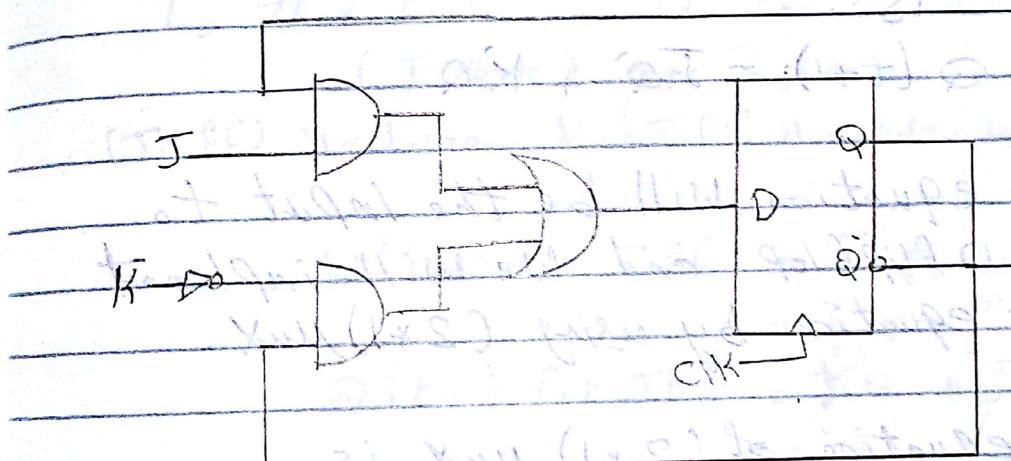~~Ex 2~~

How to implement the (TFF) by using (DFF) ?

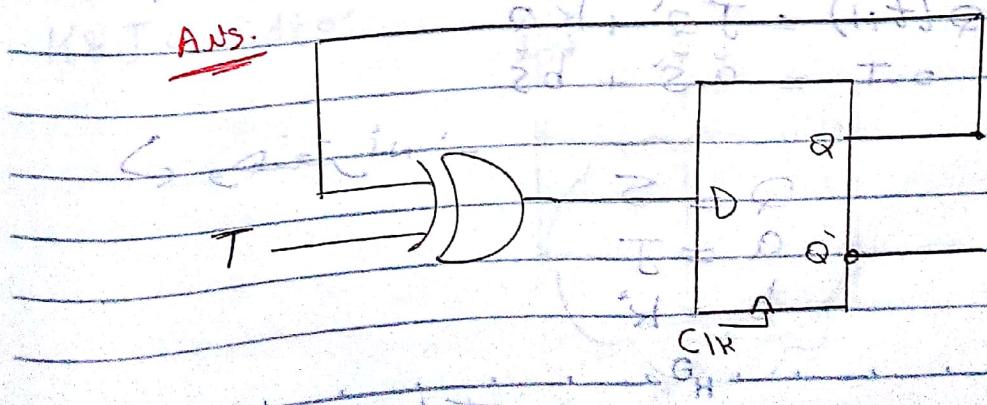Ans.

Ex 3:

No
Date

Q 5.2 in The book

→ Construct a JK Flip Flop, using D Flip Flop, a two-one Line Multiplexer, and an Inverter.

S Ans.


→ We have:-

- 1) (2x1) Mux
- 2) D Flip Flop.
- 3) an inverter

To implement the JK FF where its next eqn is:-

$$Q(t+1) = J\bar{Q} + K'Q$$

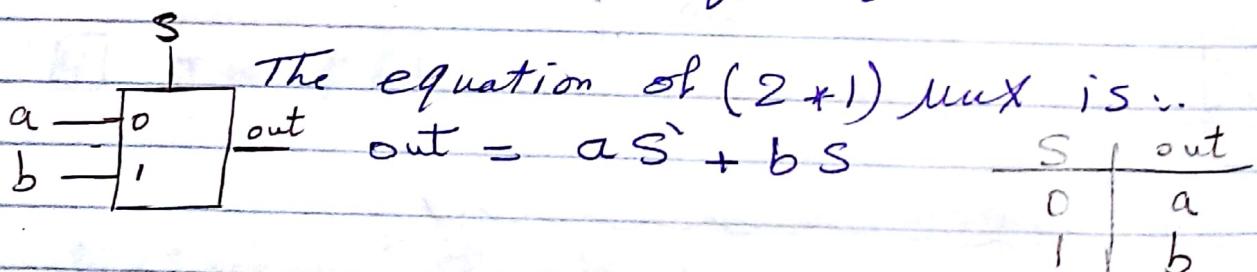→ this equation will be the input to the D Flip Flop and we will implement this equation by using (2x1) Mux.



(2x1) Mux → JK FF

$$Q(t+1) = J\bar{Q} + K'Q$$
$$out = a\bar{S} + bS'$$


$$Q = S$$

$$a = J$$

$$b = K'$$

∴ using ↗

→ The block diagram.

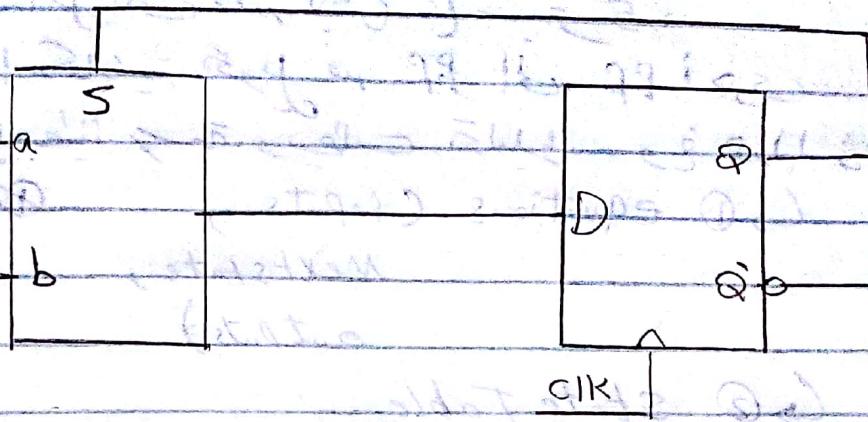

Ex:

How to Construct the Toggle Flip Flop by using JK FF?

Ans:

That will be if the inputs of JK FF
(J & K) are T.

(JK FF) \rightarrow $J = T$ & $K = T$ (T FF) \rightarrow $J = T$ & $K = T$ \rightarrow

$$Q(t+1) \text{ for } T \text{ FF} = T \oplus Q$$

$$= T'Q + TQ'$$


$$Q(t+1) \text{ for } JK \text{ FF} = J'Q + JK'$$

$$\begin{cases} J' = T \\ K = T \end{cases}$$

$$\begin{cases} J = T \\ K = T \end{cases}$$

input لـ TFF إذاً! (T FF) \rightarrow $J = T$ و $K = T$ وقت تغير عجلة (JK FF) \rightarrow

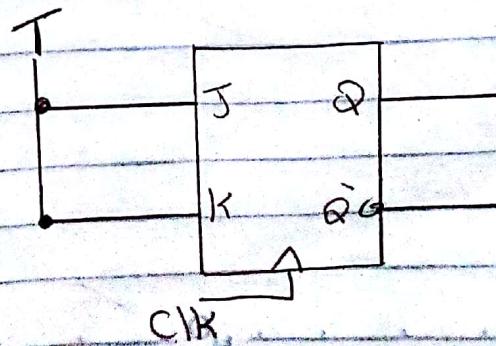$\rightarrow T =$
 $K \& J$ \rightarrow $T =$




Q5.4)

- * A PN Flip flop has fast operations, Clear to 0, no change, Complement, and Set to 1, When inputs P and N are 00, 01, 10 and 11, respectively.

- Tabulate the characteristic Table.
- Derive the characteristic equation.
- Tabulate the excitation table.
- Show how the PN Flip Flop can be converted to a D-Flip Flop.

Answer:

- The characteristic Table.

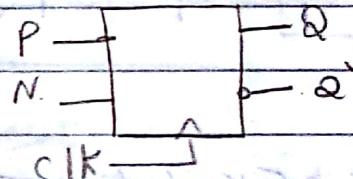

P	N	Q^*
0	0	0 (Clear to 0)
0	1	No change $\Rightarrow Q^* = Q$
1	0	Complement $\Rightarrow Q^* = \bar{Q}$
1	1	(Set to 1)


- The characteristic equation.

no table, directly

① Characteristic Table

$$Q^* = P \cdot N \bar{Q} + P \bar{N} \bar{Q} + P \bar{N} Q \quad \text{② or Transition Table}$$

→ Simplify it using K-map (3 variable)

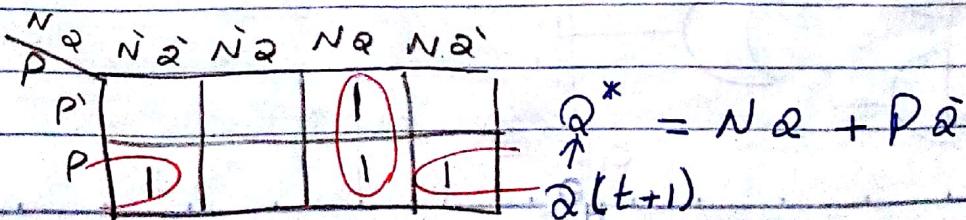

c) The Excitation Table:

~~PF will feed up to Transition Table (no role for it)~~

P	N	Q	Q*
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	1	0	0
1	1	1	1

Annotations:

- Row 1: Clear to 0
- Row 2: No change $Q^* = Q$
- Row 3: Complement $Q^* = \bar{Q}$
- Row 4: Clear to 1


The Excitation Table:

Q	Q*	P	N
0	0	0	X
0	1	1	X
1	0	X	0
1	1	X	1



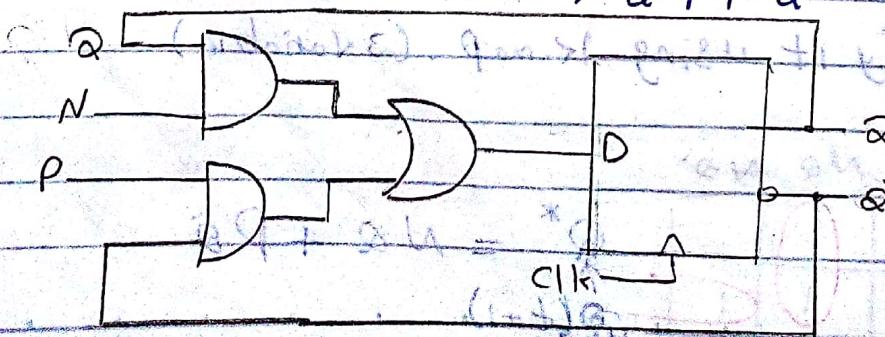d) We Can Convert PN FF to D-FF. Where:

$$Q(t+1) \text{ for } PN \text{ FF} = NQ + P\bar{Q}$$



→ (Q5.3 in Summer Exam) :-

- * A LM Flip Flop has four operations, Clear to 0, no change, Complement and Set to 1, when its inputs L and M are 00, 01, 10 and 11, respectively.
- Tabulate the characteristic table
 - Derive the characteristic equation
 - Tabulate the excitation table
 - Show how the LM flip-flop can be converted to D flip-flop

→ The same solution of the previous question put the inputs are L & M NOT N & P.

Example

Reset

- * A XY flip flop has four operations, ~~Set to 0~~, Set to 1, Change, no change, when its inputs X and Y are 00, 01, 10, 11, respectively.

- Tabulate the characteristic table.
- Derive the characteristic equation.
- Tabulate the excitation table.
- Show how the XY flip flop can be converted to D FF.

Answer:-

- The characteristic table :-

X	Y	Q^*
0	0	0
0	1	1
1	0	Change $Q^* = \bar{Q}$
1	1	No change $Q^* = Q$

$$Q^* = \bar{X}Y + X\bar{Y}\bar{Q} + XYQ$$

G H


b) The characteristic equations:

$$Q(t+1) = \bar{X}Y + X\bar{Y} + XYQ$$

\bar{Y}_2	\bar{Y}_1	\bar{Y}_2	$\bar{Y}_2 + Y_2$
X	X		Q
X			Q
X	1	1	1

$$Q(t+1) = Y_2 + \bar{X}Y + X\bar{Y}$$

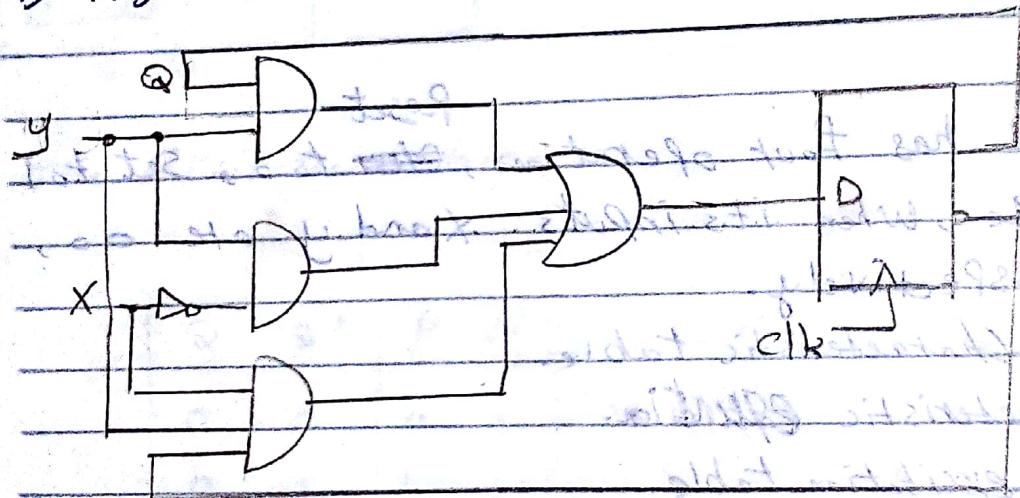d) XY flipflop can be converted to a D flipflop.



c) Excitation table:

		$Q \rightarrow Q^*$		$Q \rightarrow Q^*$	
		0	1	0	1
		$X \quad Y$		$X \quad Y$	
0	0	X	X	0	0
0	1	X	X	1	1
1	0	X	0	0	0
1	1	X	1	1	0

⇒ A Flip Flop With three inputs S, R, T , as shown.

S and R inputs behave exactly like SR FF.


While T input behaves like the toggle FF.

No more than one of these inputs may be 1 at any time

a) Show State diagram for this Flip Flop

b) Write an equation for Q^* in terms of

S, R, T and Q

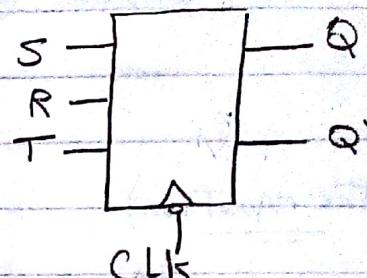

$$\overline{S}T^* + \overline{S}\overline{T} + \dots = Q^*$$

The Solution:

The Truth Table :-

S	R	T	Q	Q^*
0	0	0	0	0
0	0	0	1	①] No change
0	0	1	0	①]
0	0	1	1	0] TFF, Where $T=1$
0	1	0	0	0]
0	1	0	1	0] Reset, Where $R=1$
0	1	1	0	-] Not allowed, Where $T=1, R=1$
0	1	1	1	-]
1	0	0	0	1] (1) by 2nd (ii) opE $Q(S, Q) \leftarrow$
1	0	0	1	①] Set, Where $S=1$
1	0	1	0	-]
1	0	1	1	-]
1	1	0	0	-]
1	1	0	1	-]
1	1	1	0	-]
1	1	1	1	-]


$$q^* = \Sigma_m(1, 2, 8, 9) + \Sigma_d(6, 7, 10, 11, 12, 13, 14, 15)$$

$S R$	$S' R'$	$S R$	$S R$	$S R'$
0	4	12	8	
1	5	13	X	9
2	6	14	11	X
3	7	X	X	
4	X	X	X	X

b) The equation)

$$q^* = S + T Q' + R' T' Q$$

a) \Rightarrow The state diagram:

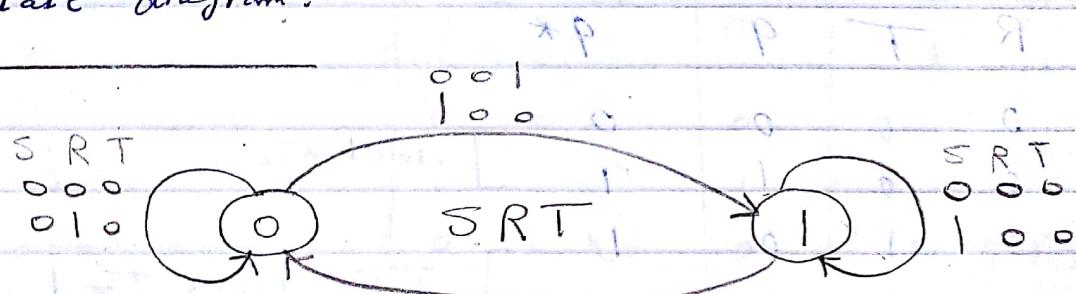

(Markovitz) book


Q5: (P. 401 Exercises) :-

→ We have a new type of flip flop, with inputs A and B.

If $A=0$, then $Q^*=B$ & if $A=1$, $Q^*=B'$

- a) Show a state diagram for this flip flop. (I)
 b) Write an equation for Q^* in terms of A, B, and Q. (II)

The Solution:

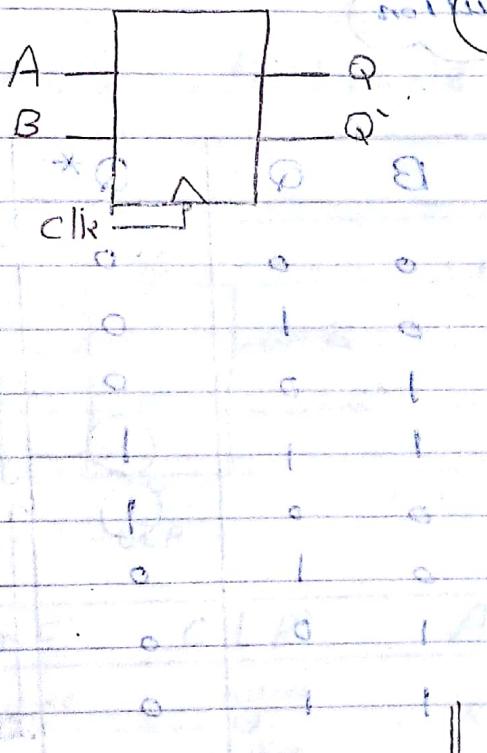


A	B	Q	Q^*
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$Q^* = B$ because "A=0"
 $Q^* = B'$ because "A=1"

(v, e) $Q^* = \sum m(2, 3, 4, 5)$

AB	$A'B'$	$A'B$	AB	AB'
Q	0	2	6	4
Q'	1	3	7	5
Q	1	0	0	1

* State diagram :-

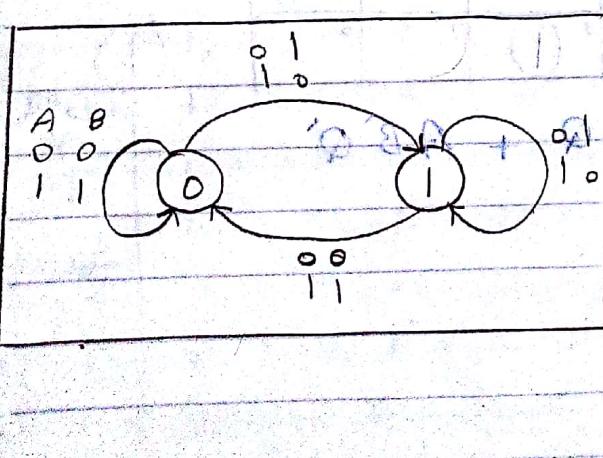

$Q^* = A'B + AB' = A \oplus B$

(The equation) $\Rightarrow Q^* = A \oplus B$


Q5.b (Final 2012):

⇒ We have a new type of a flip flop. With inputs A and B.
if $A=0$, then $Q^* = Q \bar{B}$, IF $A=1$, then $Q^* = \bar{Q} B'$

I) Show a state diagram for this flip flop.

II) Write an equation for Q^* in terms of A, B and Q.

The Solution

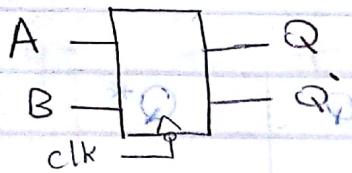


S	A	B	Q	Q^*
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
1	0	1	1	1
1	1	0	0	1
1	0	1	0	0
1	1	1	0	0
1	1	1	1	0

$$A=0 \\ \hookrightarrow Q^* = Q \bar{B}$$

$$A=1 \\ \hookrightarrow Q^* = \bar{Q} B'$$

⇒ The state diagram :-

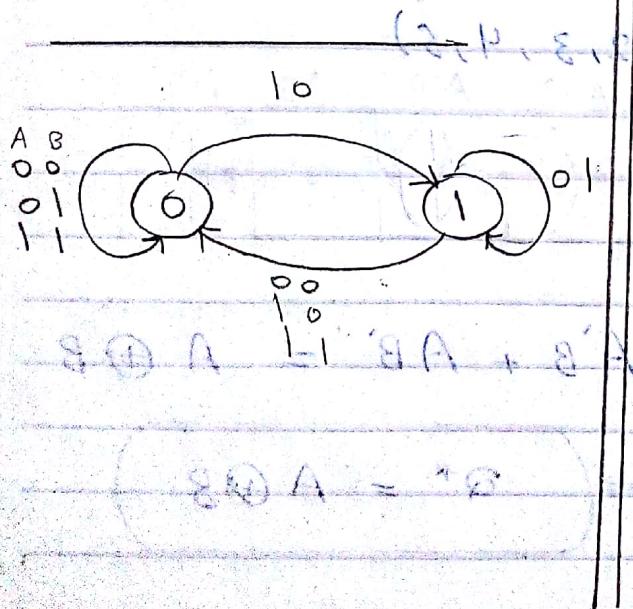


$$Q^* = \sum m(3,4)$$

AB	$A'B'$	$\bar{A}'B$	AB	$A\bar{B}'$
Q'	0	1	0	1
Q	1	0	1	0

$$Q^* = A'B'Q + A\bar{B}'Q'$$

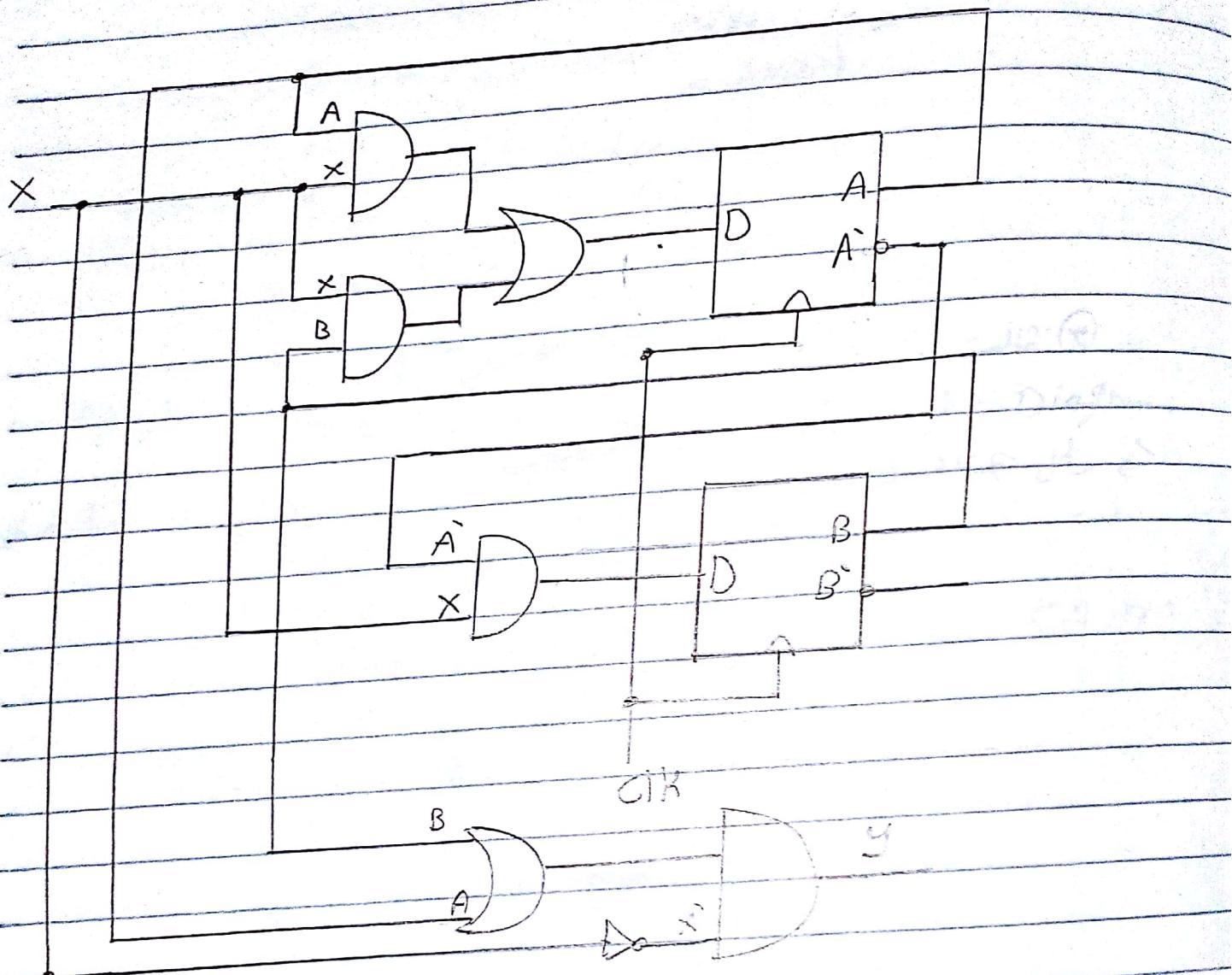Ex 5: Analyze the following sequential Circuit.



Ans.

- * The analysis of the sequential circuit is by:
 - 1) obtaining the input equations, The output equation, Next state equations.
 - 2) Constructing the State table.
 - 3) Drawing the State diagram.



III The equations ..

In D Flip Flop $\Rightarrow Q(t+1) = D$

For A flip flop ..

$$\hookrightarrow DA = AX + BX$$

$$\hookrightarrow A(t+1) = DA = AX + BX$$

For B flip flop ..

$$\hookrightarrow DB = \bar{A}X$$

$$\hookrightarrow B(t+1) = DB = \bar{A}X$$

(The output equation ..)

$$Y = X^*(A + B)$$

[2] State Table:

الجدول المترافق مع المدخلات في حالة State Table

$$A(t+1) = AX + BX$$

$$B(t+1) = \bar{A}X$$

$$Y = X^*(A + B)$$

When $X = 0$

$$A(t+1) = 0$$

$$B(t+1) = 0$$

$$Y = A + B$$

When $X = 1$

$$A(t+1) = A + B$$

$$B(t+1) = \bar{A}$$


$$Y = 0$$




The State table:-

input	Present state		next state		output
X	A	B	A*	B*	Y
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	0	1
0	1	1	0	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	1	0	0
1	1	1	1	0	0

3) The state Diagram:

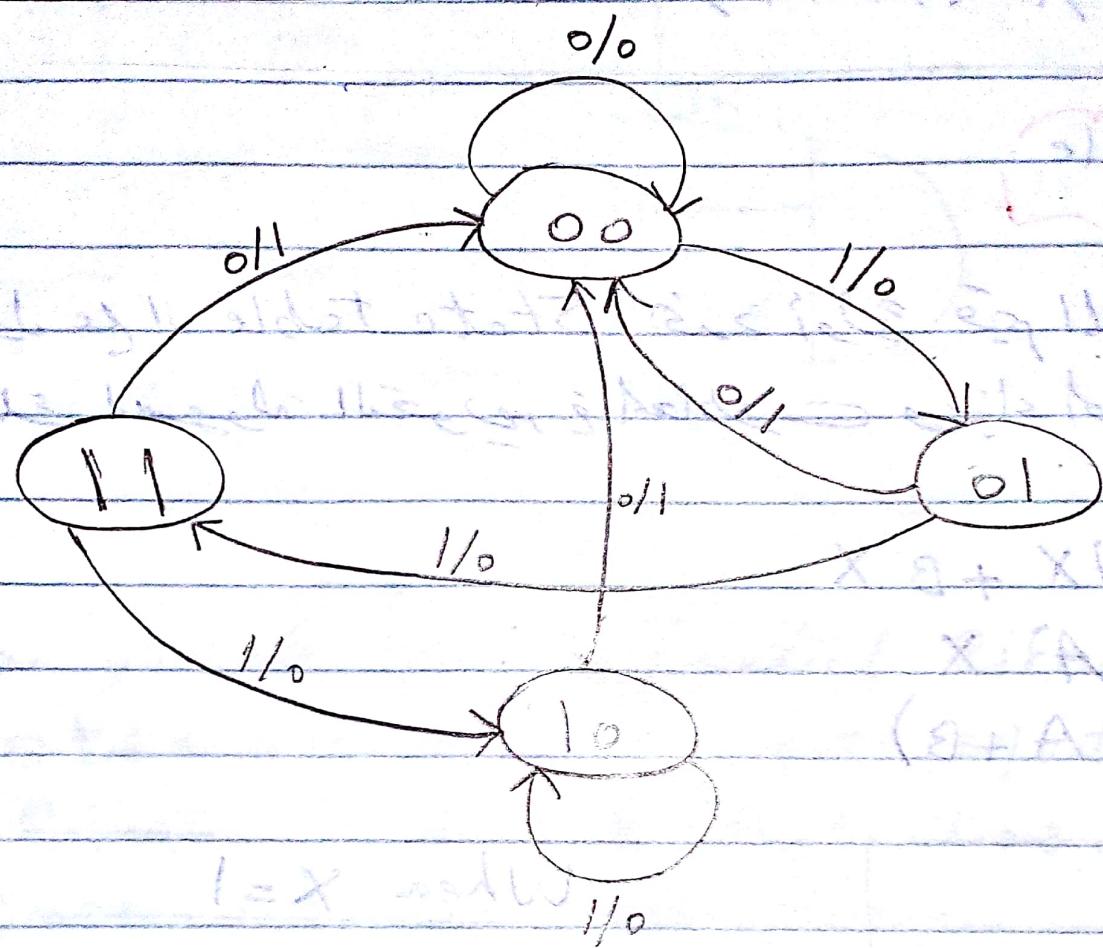

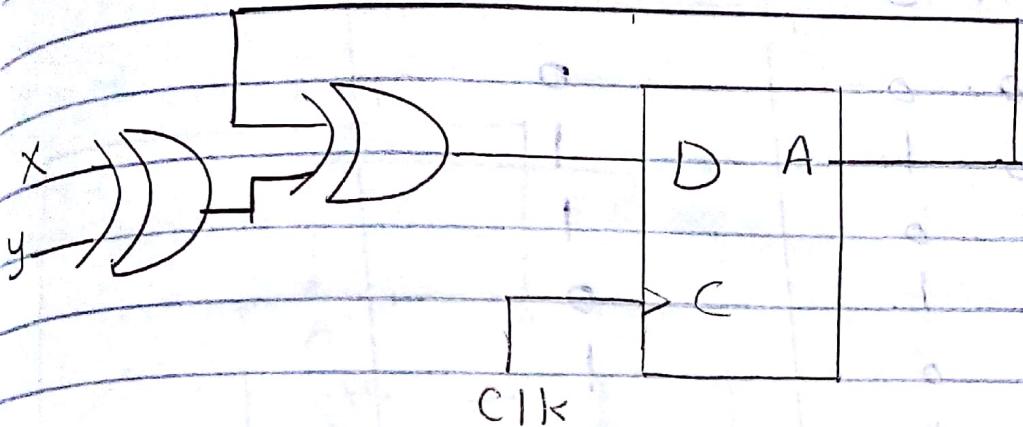~~Ex 6~~ * Analyze the following sequential Circuit.



ANS.

(1) The equations:

$$DA = (x \oplus y) \oplus A$$

$$A(t+1) = DA = x \oplus y \oplus A$$

↳ Where in D flip flop $Q(t+1) = D$

(2) The State Table:




The State table::


inputs	Present state	next state.	
x	y	A	A^*
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

③ The State Diagram:

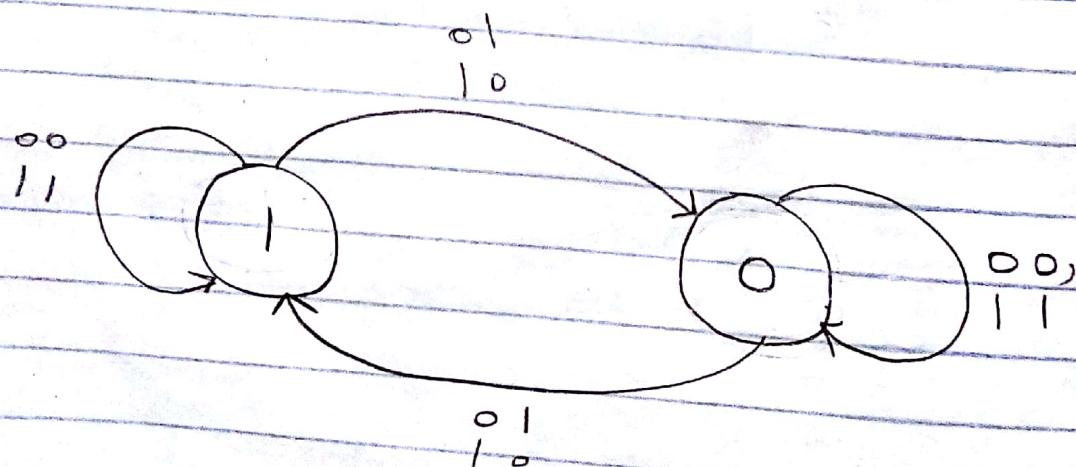State table two inputs (A) ~~وأيضاً~~ واحد (DFA) له 2
أو 3 مكونات Σ $\{0, 1\}$ \cup $\{0, 1\}$
أو 2 (state) حالات Σ حالات Σ



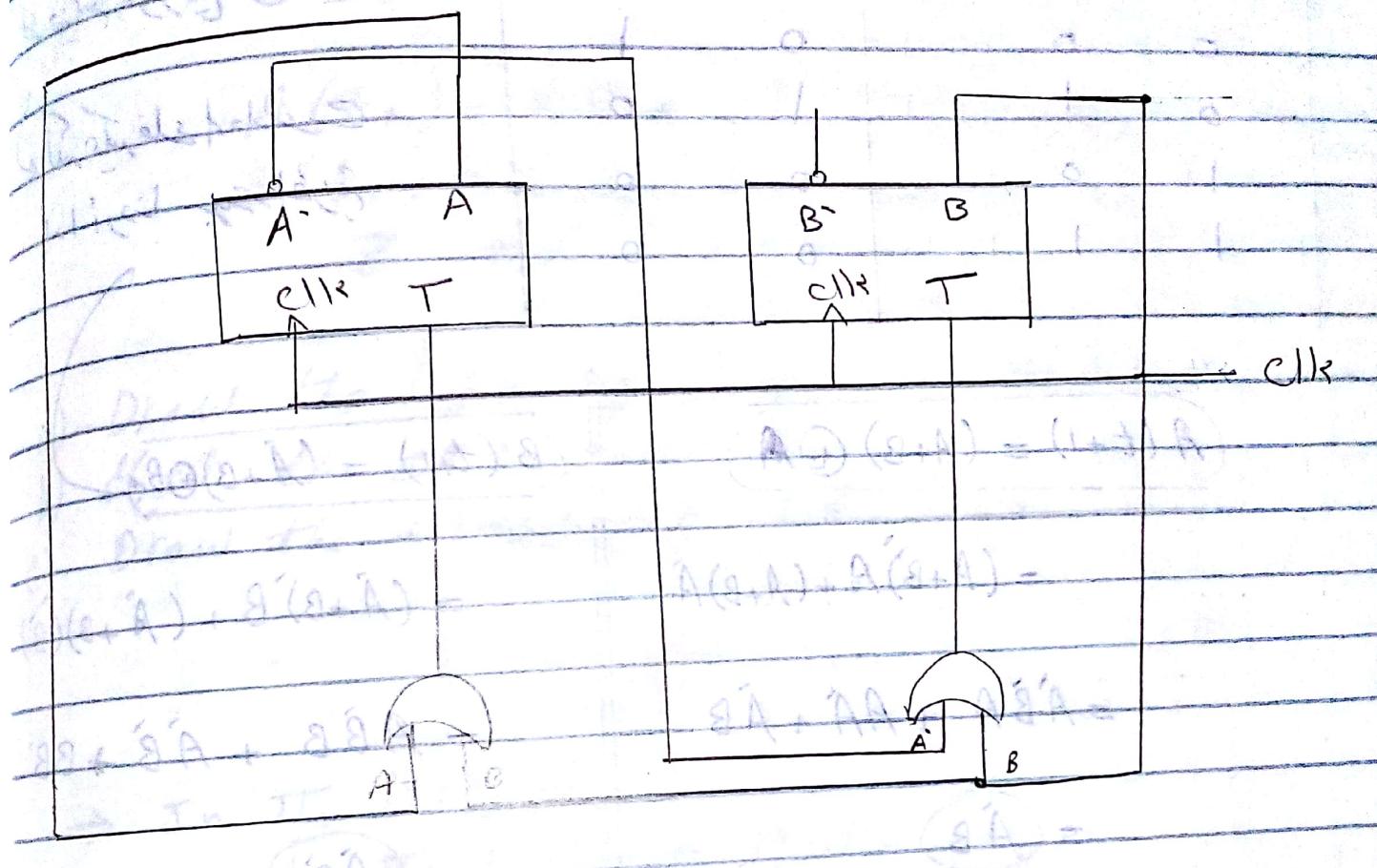X1 Derive the state table and the state diagram of the sequential circuit in the following figure.



Ans.

II The equations.

↔ The used flip flops are T-ff.

For A ff :

$$\begin{aligned} \rightarrow T_A &= A + B \\ \rightarrow Q(t+1) \Rightarrow A(t+1) &= T_A \oplus A \\ &= (A+B) \oplus A \end{aligned}$$

For B ff :

$$\begin{aligned} \rightarrow T_B &= \bar{A} + B \\ \rightarrow B(t+1) &= T_B \oplus B \\ &= (\bar{A} + B) \oplus B \end{aligned}$$

[2] The State table.

$$A(t+1) = (A+B) \oplus A$$

$$B(t+1) = (\bar{A} + B) \oplus B$$

Present state			Next state	
A	B		$A(t+1)$	$B(t+1)$
0	0	0	0	1
0	1	1	1	0
1	0	1	0	0
1	1	1	0	0

$\underline{\underline{X \oplus R}}$ \oplus $\underline{\underline{\text{نوز و زیر}}}$

$\underline{\underline{\text{عذاب خانه}}}$
 $\underline{\underline{\text{بازی خانه}}}$

$$(A(t+1)) = (A+B) \oplus A$$

$$= (A+B)A + (A+B)\bar{A}$$

$$= \bar{A}\bar{B}A + AA\bar{B} + \bar{A}\bar{B}$$

$$= \bar{A}\bar{B}$$


$$(B(t+1)) = (\bar{A} + B) \oplus B$$

$$= (\bar{A} + B)B + (\bar{A} + B)\bar{B}$$

$$= A\bar{B}B + \bar{A}\bar{B} + BB$$


$$= \bar{A}\bar{B}$$

[3] The state diagram.

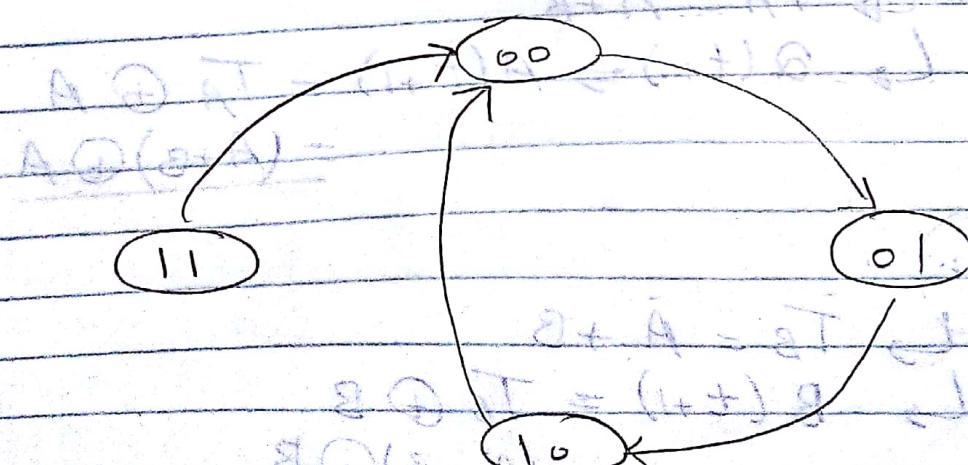

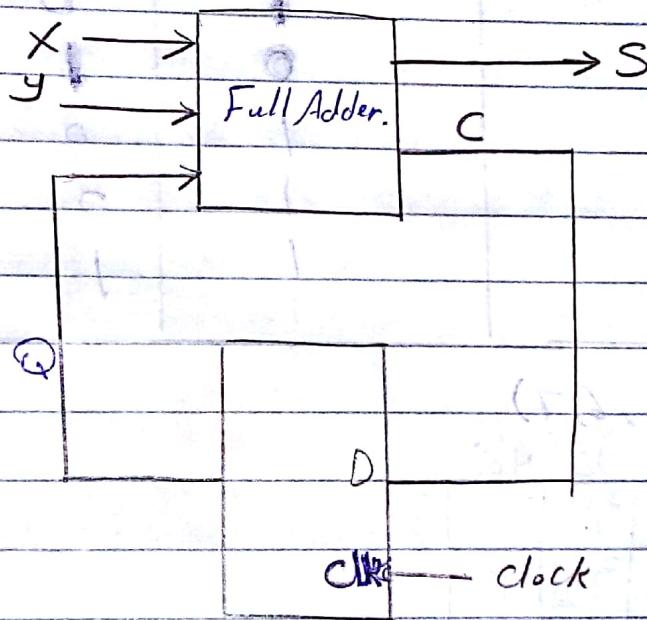Q4 : Sheet 4 - Q (5-7)

→ A sequential circuit has one D flip-flop Q , two inputs x and y , and one output S . It consists of a full-adder circuit connected to a D flip-flop, as shown in the following figure. Derive the state table and the state diagram of the sequential circuit.



Ans

→ From the Diagram :-

$$D = C \text{ [Cont]}$$

The next state of DFF is $\boxed{Q^* = \bar{D}}$

So:-

$$Q^* \text{ or } Q(t+1) = D = C$$



The state table:-

Inputs	Present state	Next state $Q^* = \text{Cout}$	Output S
X	Y	Q	
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


$$Q^* = \Sigma m(3, 5, 6, 7)$$

	y_Q	$y_{\bar{Q}}$	y_Q	$y_{\bar{Q}}$	y_Q
x	0	1	3	1	2
\bar{x}	4	5	7	0	6

$$Q(t+1) = y_Q + xQ + xy$$


$$S = x \oplus y \oplus Q \leftarrow$$

The State Diagram:

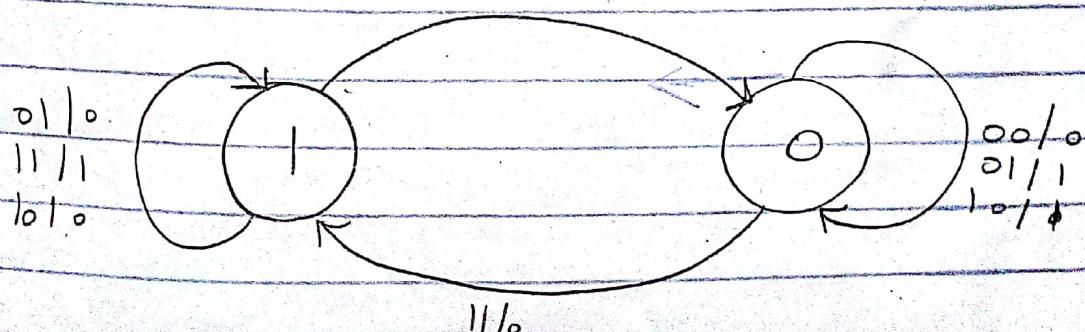

Q. 8 (2009)

Given the following circuit:

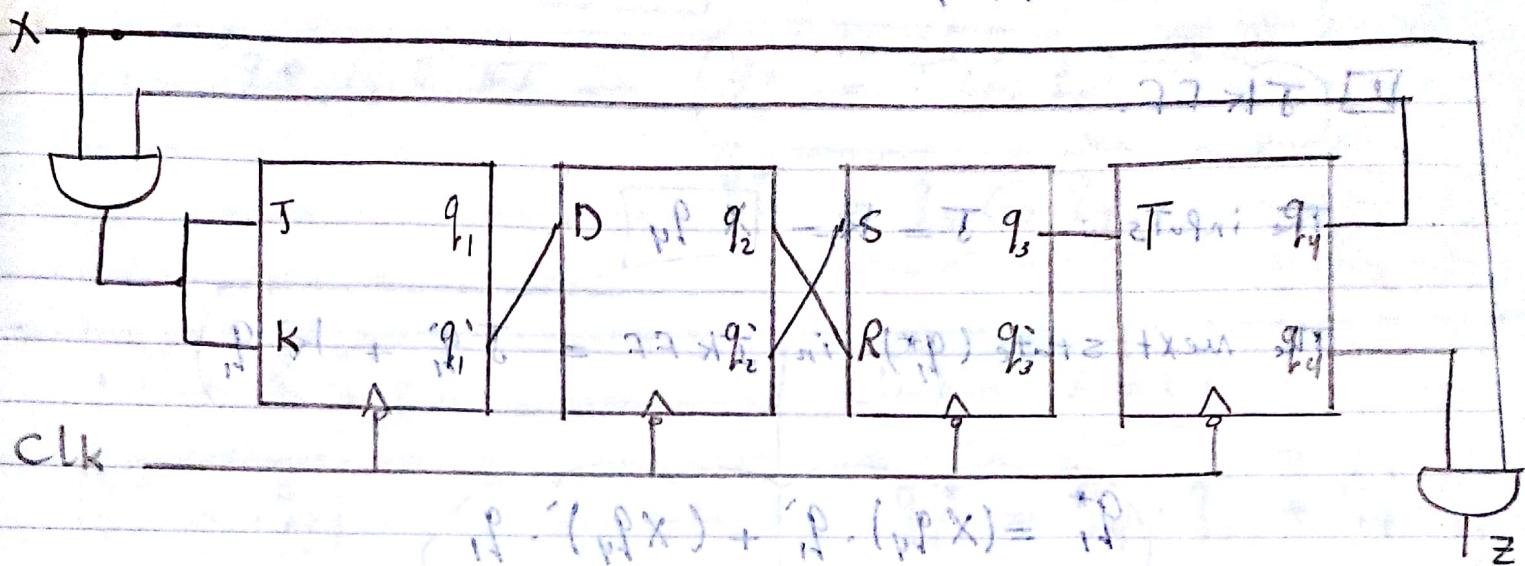

a) The state model is (Mealy model)

because, the output ($Z = (X \cdot q_4)$) depends on the state and the input.

b) Build the state table:

$$ip = sp$$



$$sp = R \quad ip = Z$$

$$ip = R + Z \leftarrow 7783 \text{ in } sp$$

From the design:

↳ we have 4 flip flops.

① JK FF.

The inputs: $J = K = X q_4$

The next state (q_1^*) in $Jk\text{FF} = J q_1 + K \bar{q}_1$

$$q_1^* = (X q_4) \cdot q_1 + (X q_4) \cdot \bar{q}_1$$

② D FF

The inputs: $D = q_1$

q_2^* in DFF $\Rightarrow q_2^* = D$

$$q_2^* = q_1$$

③ SR FF

The inputs: $S = q_2$, $R = q_2$

q_3^* in SR FF $\Rightarrow S + R \bar{q}_3$

$$q_3^* = q_2 + q_2 \bar{q}_3 = q_2 (1 + q_3)$$

$$q_3^* = q_2$$

4) TFF:

The inputs :

$$T = q_3$$

$$q^* \text{ in TFF} \Rightarrow q_4^* = T \oplus q_4$$

$$q_4^* = q_3 \oplus q_4$$

When $x = 0$

$$q_1^* = q_1$$

$$q_2^* = q_1$$

$$q_3^* = q_2$$

$$q_4^* = q_3 \oplus q_4$$

$$Z = 0$$

When $x = 1$

$$q_1^* = q_4 \cdot q_1 + q_4 \cdot q_1$$

$$q_1^* = (q_4 \oplus q_1)$$

$$q_2^* = q_1$$

$$q_3^* = q_2$$

$$q_4^* = q_3 \oplus q_4$$

$$Z = q_4$$

⇒ The State table : \Rightarrow


The state table.

$$Z = X \cdot q_4$$

Present State	Next State	Output (Z)
$q_1 \ q_2 \ q_3 \ q_4$	$q_1^* \ q_2^* \ q_3^* \ q_4^*$ $x=1$ $q_1^* \ q_2^* \ q_3^* \ q_4^*$	$x=0 \quad x=1$ $Z = 0 \quad Z = q_4$
0 0 0 0	0 1 1 0 0 1 1 0	0 1
0 0 0 1	0 1 1 1 1 1 1 1	0 0
0 0 1 0	0 1 1 1 0 1 1 1	0 1
0 0 1 1	0 1 1 0 1 1 1 0	0 0
0 1 0 0	0 1 0 0 0 1 0 0	$0 = 0$
0 1 0 1	0 1 0 1 1 1 0 1	0 0
0 1 1 0	0 1 0 1 0 1 0 1	0 1
0 1 1 1	0 1 0 0 1 1 0 0	0 0
1 0 0 0	1 0 1 0 1 0 1 0	$0 = 1$
1 0 0 1	1 0 1 1 0 0 1 1	0 0
1 0 1 0	1 0 0 1 1 0 1 1	$0 = 1$
1 0 1 1	1 0 1 0 0 0 1 0	0 0
1 1 0 0	1 0 0 0 1 0 0 0	$0 + 0 = 0$
1 1 0 1	1 0 0 1 0 0 0 1	0 0
1 1 1 0	1 0 0 1 1 0 0 1	0 1
1 1 1 1	1 0 0 0 0 0 0 0	$0 + 0 = 0$

← state table

Q1) Quiz 3 (2012) :-

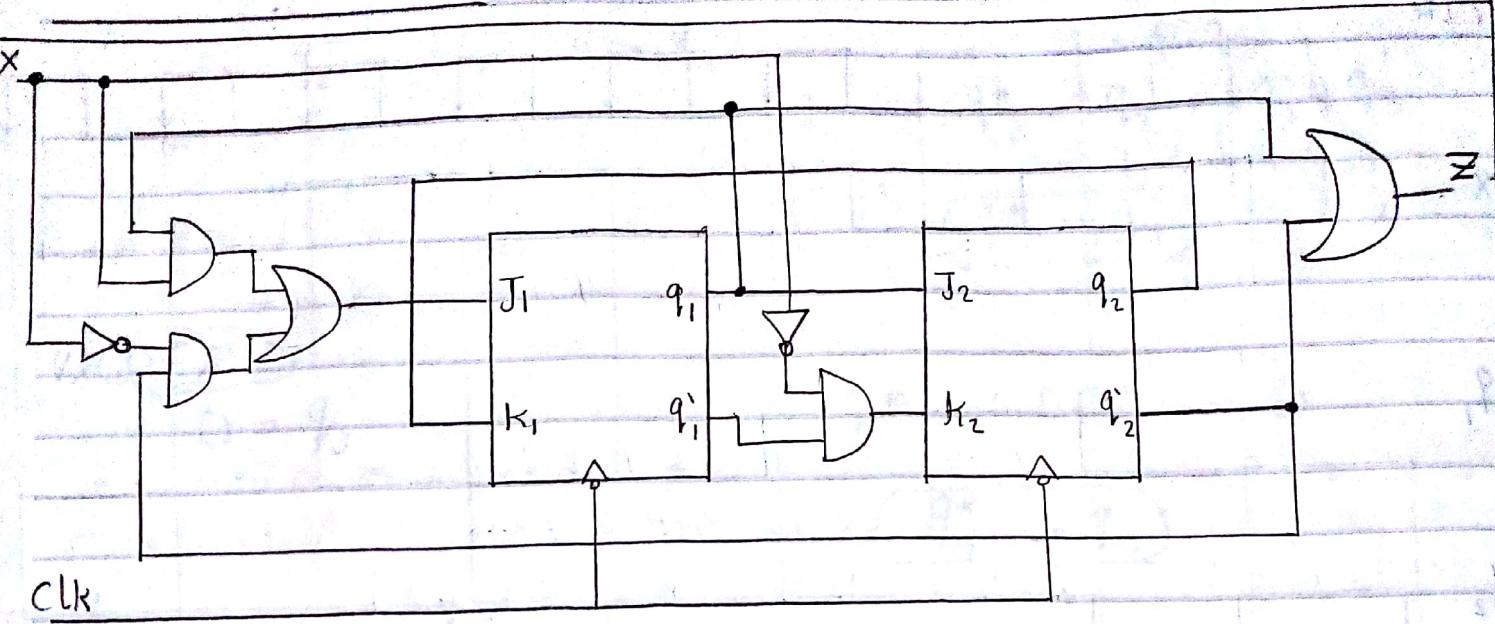

→ Obtain the high level description of the following sequential network, and complete the timing diagram:-

The Solution:-

- * This design is "Moore Model" Where :
The output ($Z = q_1 + q_2'$) depends only on the state.
- * From the design, there are two Flip Flops \Rightarrow (JK FF) :-

The inputs :-

JK FF1 :-

$$J_1 = X q_1 + X' q_2'$$

$$K_1 = q_2$$

JK FF2 :-

$$J_2 = q_1$$

$$K_2 = X' q_1$$

* The next state in JK FF: $= (J\bar{q} + \bar{K}q)$

$$q_1^* = J_1 q_1 + K_1 \bar{q}_1$$

$$= (\cancel{X \cdot q_1} + \cancel{X \cdot \bar{q}_2}) \cdot \bar{q}_1 + (\bar{q}_2) q_1$$

$$= q_2 (\cancel{X \cdot q_1} + q_1) = q_2 (\cancel{X} + q_1)$$

$$q_1^* = q_2 (X + q_1)$$

$$q_2^* = J_2 q_2 + K_2 \bar{q}_2$$

$$= q_1 q_2 + (X \cdot q_1) q_2$$

$$= q_1 q_2 + (X + q_1) q_2$$

$$= q_1 q_2 + X q_2 + q_1 q_2$$

$$= q_1 (q_2 + q_2) + X q_2$$

$$q_2^* = q_1 + X q_2$$



$$q_1^* = q_2(x) + q_1$$

$$q_2^* = q_1 + \times q_2$$

When $x = 0$

$$q^+|_{x=0} = q_2'$$

$$q_2^+ \Big|_{x=0} = q_1$$

When $x = 1$


$$(q_1^*)_{x=1} = q_1 q_2$$

$$\frac{q_1^*}{2} + \frac{q_2^*}{2} = q_1 + q_2$$

* The state table:


Present state		Next state		Output
q_1	q_2	q_1^*	q_2^*	Z
0	0	1	0	1
0	1	0	1	0
1	0	1	1	1
1	1	0	1	1

* The State Diagram:

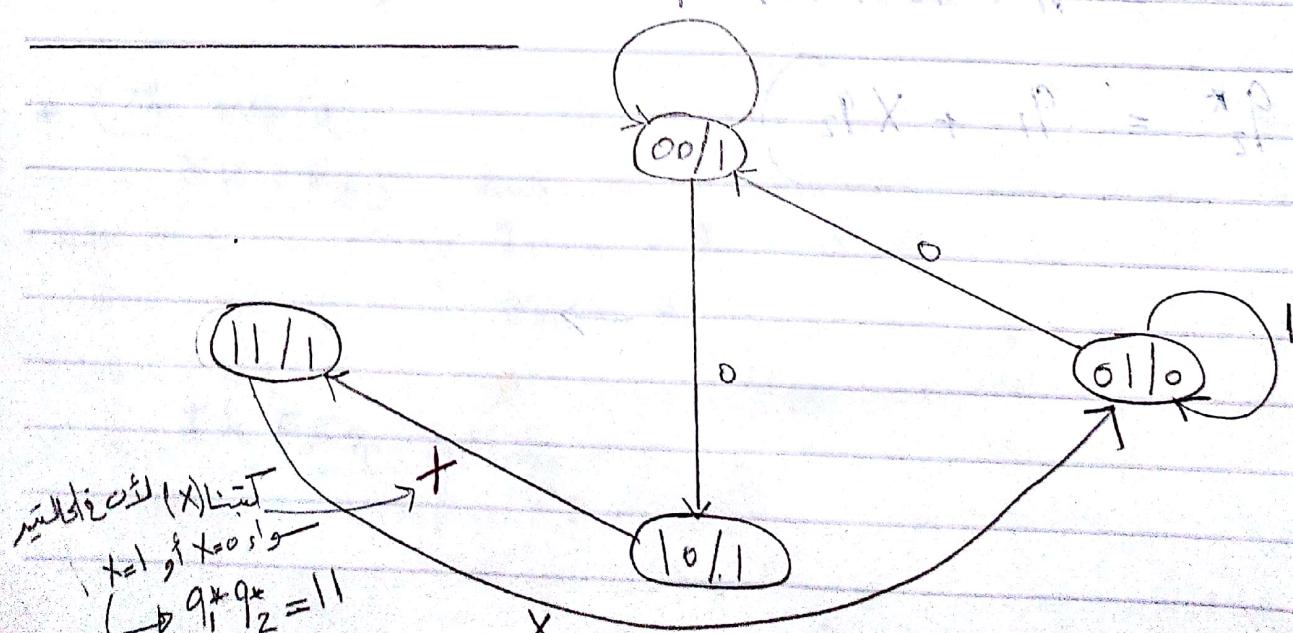

Q7 (June 2010) :

Given the following circuit:

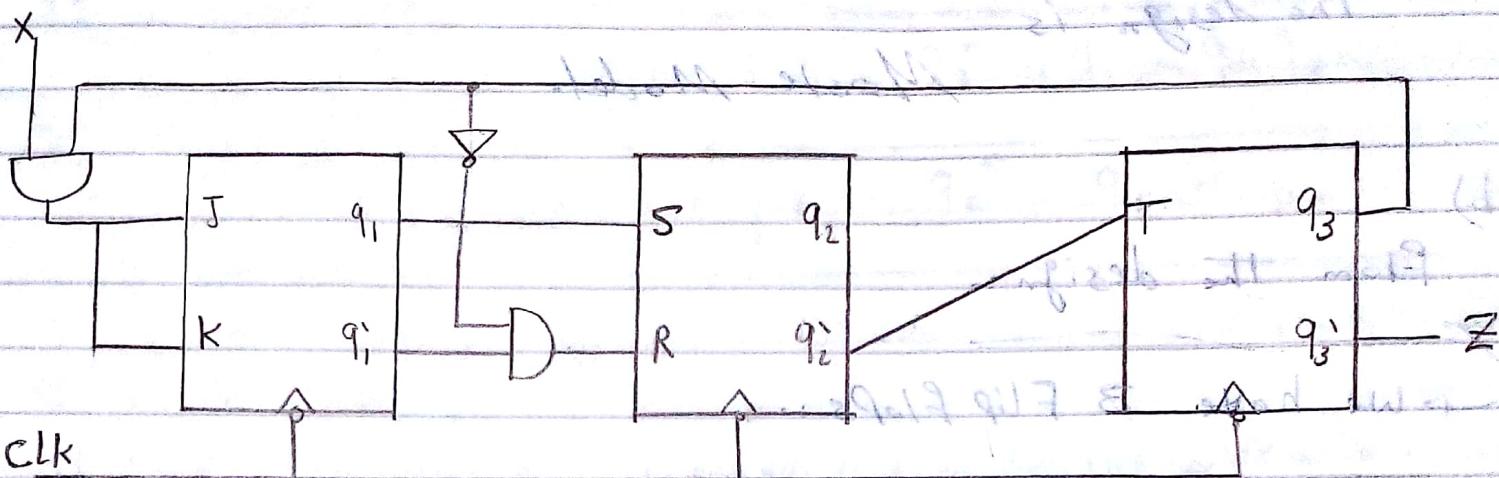

a) State the design model

b) Build the state table

The Solution:-

a) The output ($Z = q_3$) depends only on the state, So
The design is Moore Model.

b) From the design:-

→ We have 3 Flip Flops :-

① JK FF

$$J = K = X q_3$$

$$q_{JK}^* = J q_i + K' q_i$$

$$= X q_3 q_i + (X q_3)' q_i$$

$$(q_1^* = X q_3 q_i + (X + q_3)' q_i)$$

$$q_{SR}^* = S + R' q_2$$

$$\begin{aligned} q_2^* &= q_1 + (q_1 q_3)' q_2 \\ &= q_1 + (q_1 + q_3) q_2 \end{aligned}$$

$$= q_1 + q_1 q_2 + q_3 q_2$$

$$(q_2^* = q_1 + q_3 q_2)$$

③ T FF

$$q_3^* = T \oplus q_3$$

$$(q_3^* = q_2 \oplus q_3)$$

$$T = q_2$$

When $X = 0$

$$q_1^* = q_1$$

$$q_2^* = q_1 + q_2 q_3$$

$$q_3^* = q_2 \oplus q_3$$

When $X = 1$

$$q_1^* = q_3 q_1 + \bar{q}_3 q_1$$

$$q_1^* = q_1 \oplus q_3$$

$$q_2^* = q_1 + q_2 q_3$$

$$q_3^* = q_2 \oplus q_3$$

The State table:

Present State q_1 q_2 q_3	Next State		Z
	$X = 0$ q_1^* q_2^* q_3^*	$X = 1$ q_1^* q_2^* q_3^*	
0 0 0	0 0 1	0 0 1	1
0 0 1	0 0 0	1 0 0	0
0 1 0	0 0 0	0 1 0	1
0 1 1	0 1 1	1 1 1	0
1 0 0	1 1 1	1 1 1	1
1 0 1	1 1 0	0 1 0	0
1 1 0	1 1 0	1 1 0	1
1 1 1	1 1 1	0 1 1	0